



Algoritmos y programación


compuertas logicas

Alejandro Bacelis Eguiza

Ingeniería en TI y negocios digitales


00623074

Circuito 1

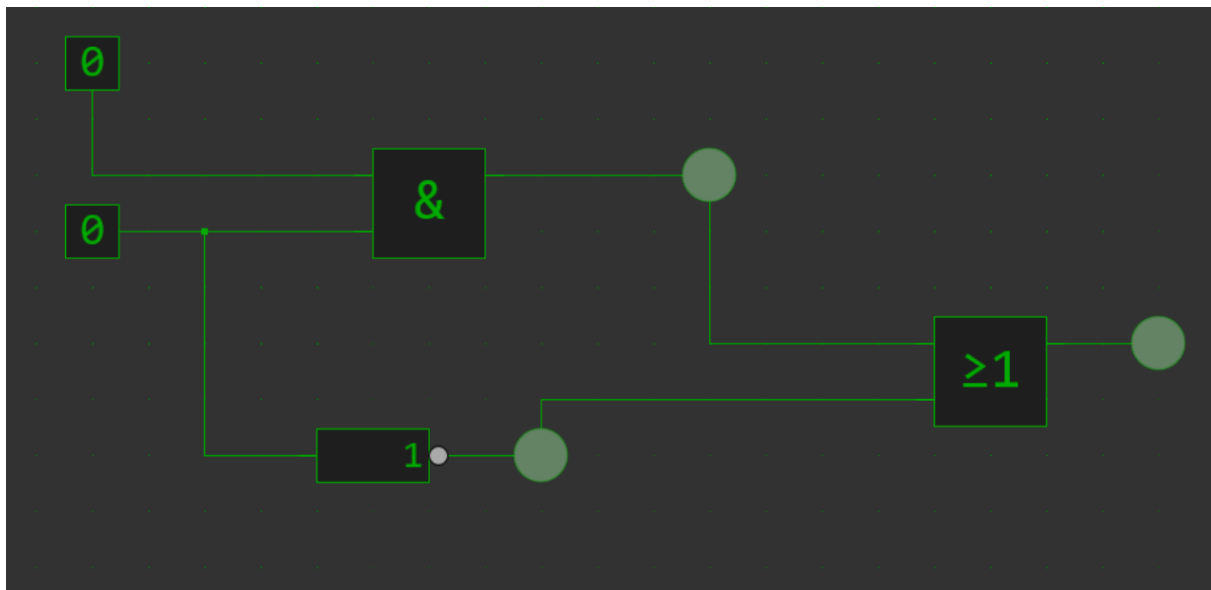


p	q	p AND q	NOT q	(p AND q) OR (NOT q)
V	V	v	f	v
V	F	f	v	v
F	V	f	f	f
F	F	f	v	v

Circuito 2

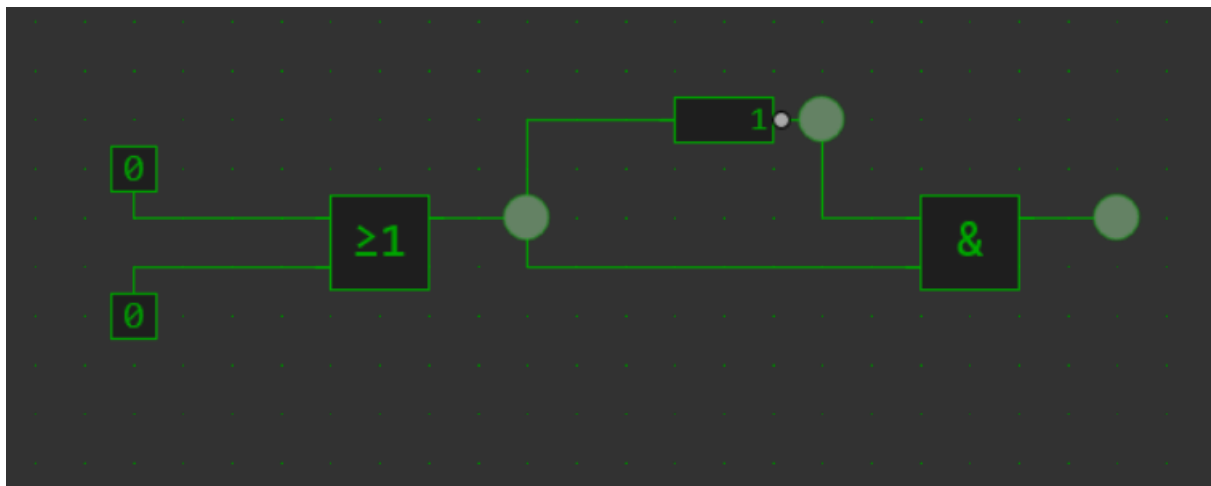


p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	v	f	f
V	F	v	f	f
F	V	v	f	f
F	F	f	v	f

Circuito 3

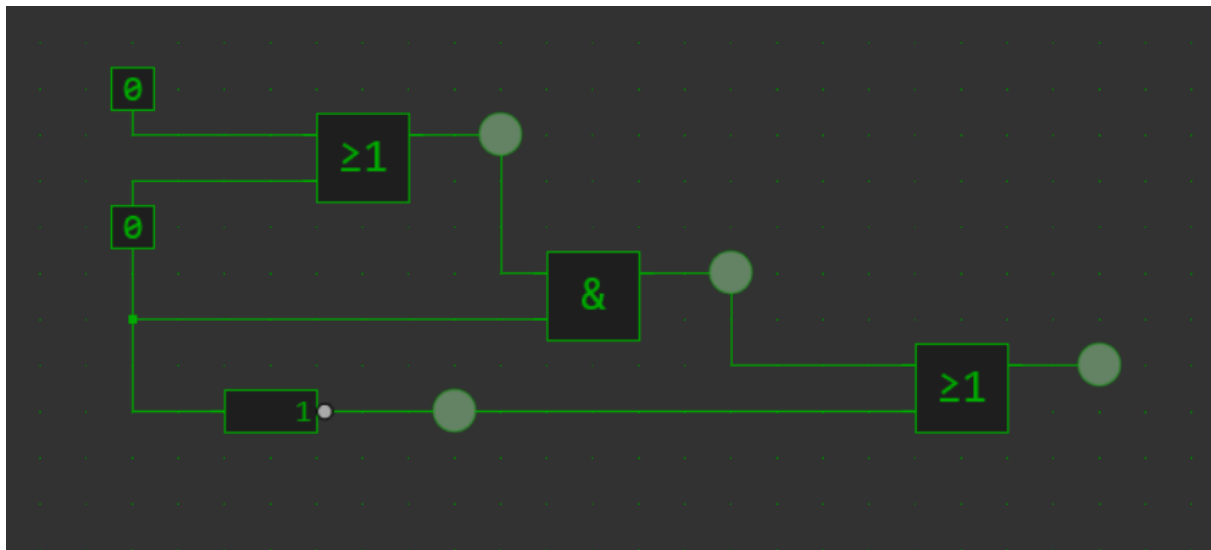

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] OR (NOT q)
V V	v	v	f	v
V F	v	f	v	v
F V	v	v	f	v
F F	f	f	v	v

Circuito 4

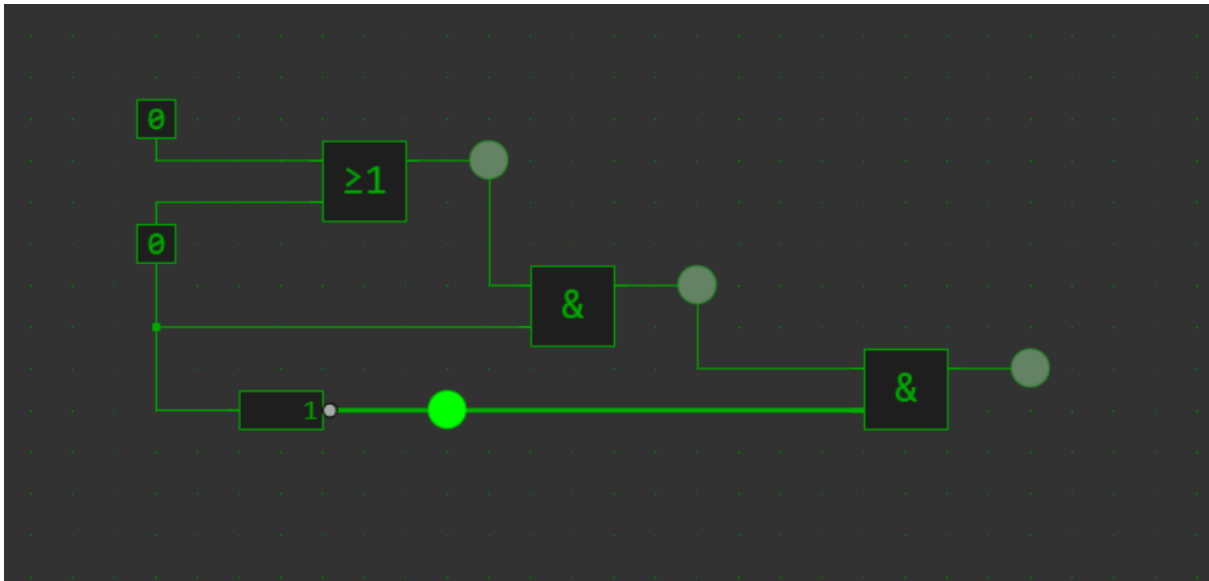

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] AND (NOT q)
V V	v	v	f	f
V F	v	f	v	f
F V	v	v	f	f
F F	f	f	v	f